
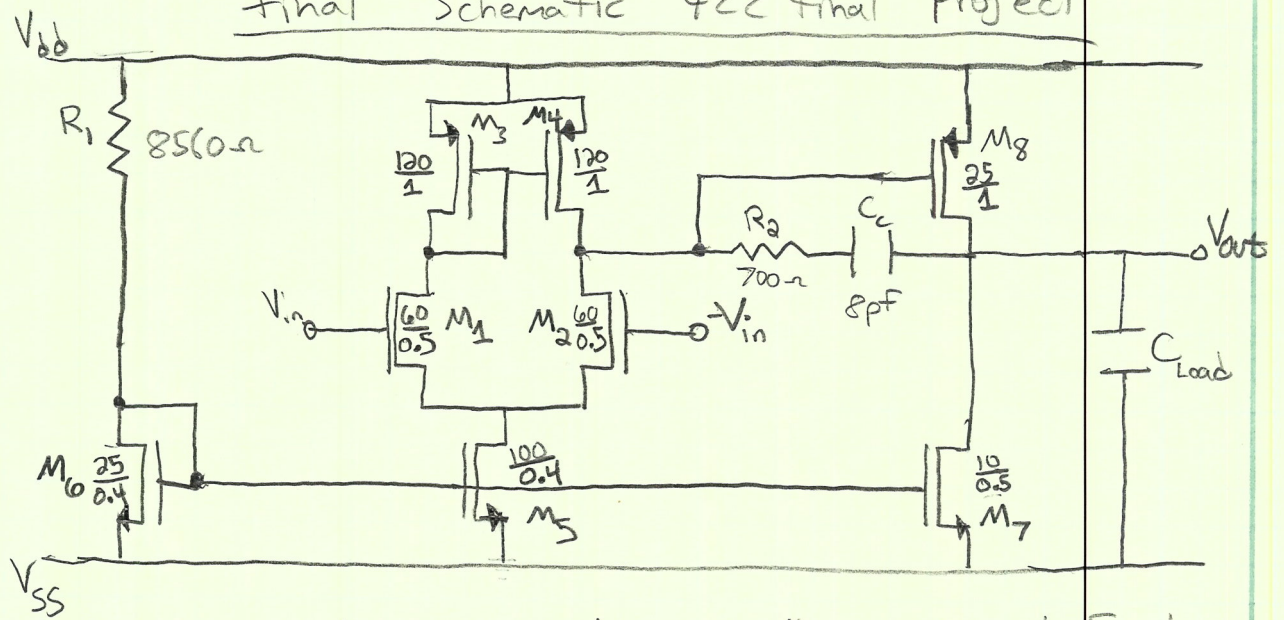


# Final Schematic 422 Final Project

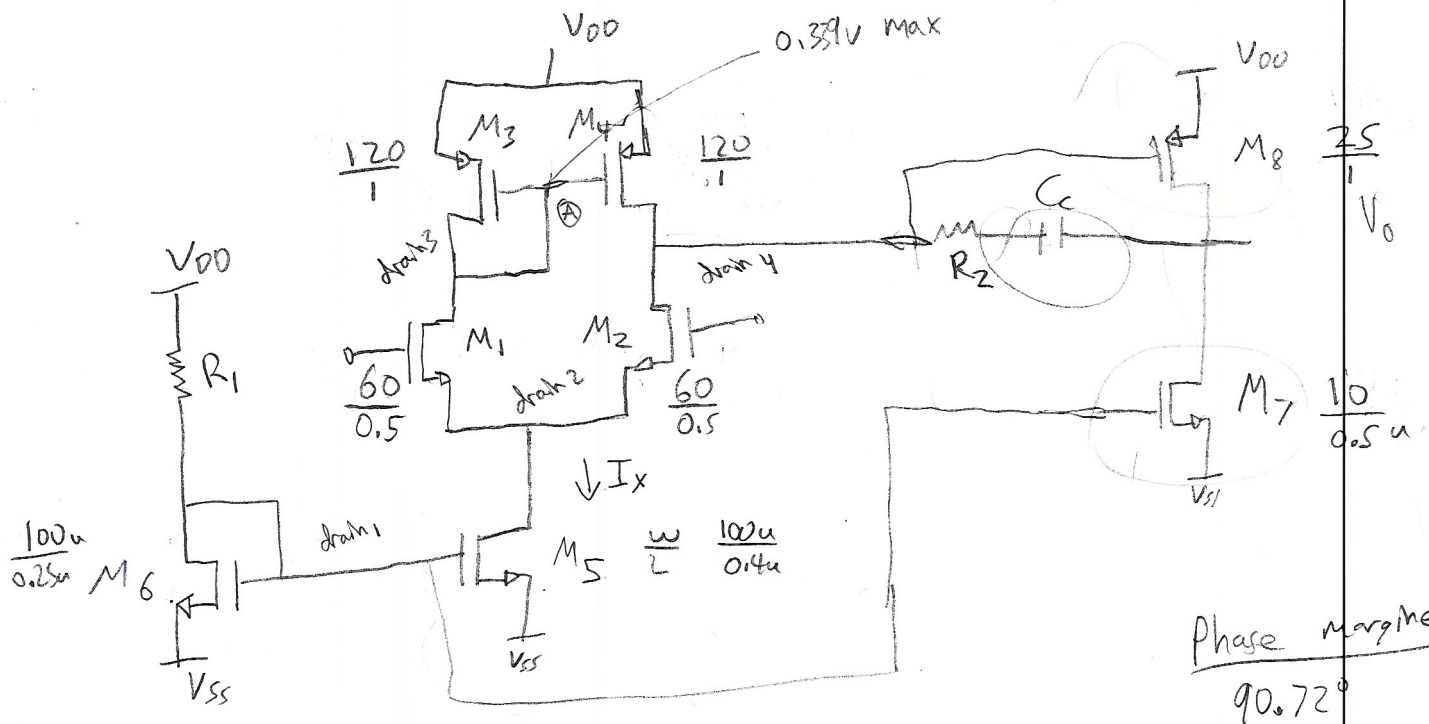

look at this Schematic the others are not Final



$$I_X = 600 \mu A$$

$$r_1 = \frac{1.16614 V}{600 \mu A} = \boxed{8560 \Omega}$$

$$\frac{1}{g_{m4}}$$

$$\frac{M_6}{M_8}$$

Makes lengths larger.

To calculate  $R_2$  I am using the same topology as in the notes. using the  $\frac{1}{g_{m4}}$

$$g_{m4} = \sqrt{2 K_n' \left(\frac{W}{L}\right) I_D}$$

to cancel out one of the poles.

$$I_D = 300 \mu A$$

$$K_n' = 235 \times 10^{-6} \frac{A}{V^2}$$

$$\left(\frac{W}{L}\right) = 120 \text{ Since } \begin{matrix} W = 60u \\ L = 0.5u \end{matrix}$$

$$g_{m4} = \sqrt{2 (235 \times 10^{-6}) (120) (300 \times 10^{-6})}$$

$$g_{m4} \approx 4.11 \text{ mS}$$

$$\frac{1}{g_{m4}} \approx 243 \Omega$$

$$R_2 \text{ needs } > 243 \Omega$$


$$\text{Now using } W_z = \frac{1}{C_c \left\{ \frac{1}{g_{m2}} - R_2 \right\}}$$

chose 8 pF for  $C_c$

Page 2

Continuing from page 1
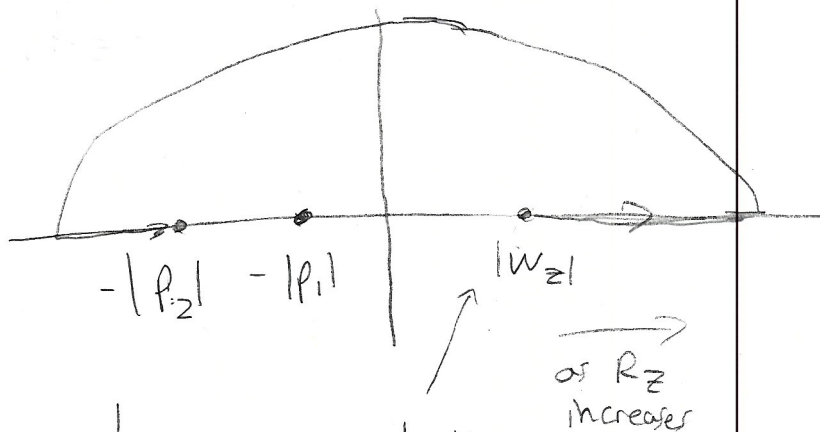
$$W_z = \frac{1}{8pf \left\{ \frac{1}{4.11ns} - R_z \right\}}$$



$$W_z = \frac{1}{8pf(243-700)}$$

$W_z = -2.73 \times 10^8$   
pushed us to the left.

at this point  $R_z \approx 243 \Omega$


So we chose 700  $\Omega$   
which pushed our  
Zero to the LHS

Canceling with one of  
the poles.



$$L \geq 0.18 \mu\text{m}$$
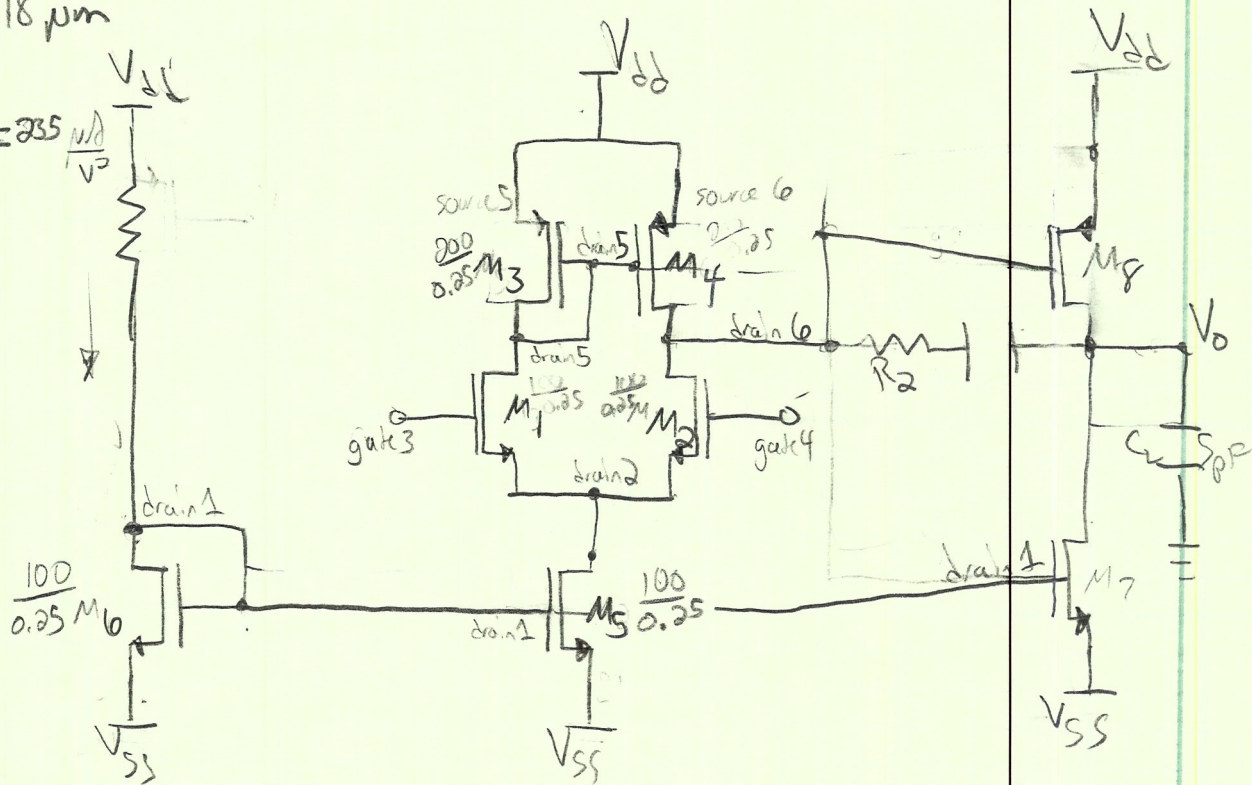
$$\text{Assume } k_n' = 235 \frac{\mu\text{A}}{\text{V}^2}$$



$$V_{dd} - V_{ov_{M8}} = V_{o_{max}}$$

$$V_{ov_{M8}} = \sqrt{\frac{2I_D}{k_p' \left(\frac{W}{L}\right)}} = \sqrt{\frac{2(53.35 \times 10^{-6})}{(235 \times 10^{-6}) \left(\frac{25}{1}\right)}} = 0.135 \text{ V}$$

$$V_{o_{max}} = 0.9 - 0.135 \text{ V} = 0.765 \text{ V}$$

$$V_o - V_{ov_{M7}} = -0.9 \text{ V}$$

$$V_{o_{min}} = V_{ov_{M7}} - 0.9 \text{ V}$$

$$V_{ov_{M7}} = \sqrt{\frac{2I_D}{k_n' \left(\frac{W}{L}\right)}} = \sqrt{\frac{2(53.35 \times 10^{-6})}{(235 \times 10^{-6}) \left(\frac{10}{0.5}\right)}} = 0.151 \text{ V}$$

$$V_{o_{min}} = -0.749 \text{ V}$$